

Experiment No. 4.1B

Design and implement a 2:1 MUX, 4:1 MUX and 8:1 MUX circuit in VHDL using Data Flow/ Behavioural Model.


Objective:

Design and implement a 4:1 MUX circuit in VHDL using Behavioural Model.

Theory:

A multiplexer is a device that selects one of several analog or digital input signals and forwards the selected input into a single line. A mux has 2^n inputs with n selection lines and it gives one output. A mux is also called a data selector.

Circuit diagram:

 

Truth table:

Data Input	Select Inputs		Outputs			
D	S_1	S_0	Y_3	Y_2	Y_1	Y_0
D	0	0	0	0	0	D
D	0	1	0	0	D	0
D	1	0	0	D	0	0
D	1	1	D	0	0	0

VHDL Source Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX_4_1 is
    Port ( a : in  STD_LOGIC ;
          b : in  STD_LOGIC ;
          c : in  STD_LOGIC ;
          d : in  STD_LOGIC ;
          s0 : in  STD_LOGIC ;
          s1 : in  STD_LOGIC ;
          z : out STD_LOGIC);
end MUX_4_1;

architecture Behavioral of MUX_4_1 is
begin
    process (A,B,C,D,S0,S1) is
        begin
            if (S0 ='0' and S1 = '0') then
                Z <= A;
            elsif (S0 ='1' and S1 = '0') then
                Z <= B;
            elsif (S0 ='0' and S1 = '1') then
                Z <= C;
            else
                Z <= D;
            end if;
        end process;
    end Behavioral;
```

VHDL TestBench Code:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY TESTMUX4X1 IS
END TESTMUX4X1;

ARCHITECTURE behavior OF TESTMUX4X1 IS

    COMPONENT MUX_4_1
    PORT(
        A : IN  std_logic;
        B : IN  std_logic;
        C : IN  std_logic;
        D : IN  std_logic;
        S0 : IN  std_logic;
        S1 : IN  std_logic;
        Z : OUT std_logic
```

```
);  
END COMPONENT;  
  
signal A : std_logic := '0';  
signal B : std_logic := '0';  
signal C : std_logic := '0';  
signal D : std_logic := '0';  
signal S0 : std_logic := '0';  
signal S1 : std_logic := '0';  
  
signal Z : std_logic;  
  
BEGIN  
  
    uut: MUX_4_1 PORT MAP (  
        A => A,  
        B => B,  
        C => C,  
        D => D,  
        S0 => S0,  
        S1 => S1,  
        Z => Z  
    );  
  
    stim_proc: process  
    begin  
        A <= '1';  
        B <= '0';  
        C <= '1';  
        D <= '0';  
  
        S0 <= '0';  
        S1 <= '0';  
        wait for 100 ns;  
        S0 <= '1';  
        S1 <= '0';  
        wait for 100 ns;  
        S0 <= '0';  
        S1 <= '1';  
        wait for 100 ns;  
        S0 <= '0';  
        S1 <= '1';  
        wait for 100 ns;  
  
    end process;  
  
END;
```

Test Bench Waveform:

