

## Design and implement 1:8 DEMUX circuit in VHDL using Behavioural Architecture:

### Truth Table:

| DIN | SEL (S2 S1 S0) | D0 | D1 | D2 | D3 | D4 | D5 | D6 | D7  |
|-----|----------------|----|----|----|----|----|----|----|----------------------------------------------------------------------------------------|
| 0   | 000            | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0                                                                                      |
| 1   | 000            | 1  | 0  | 0  | 0  | 0  | 0  | 0  | 0                                                                                      |
| 1   | 001            | 0  | 1  | 0  | 0  | 0  | 0  | 0  | 0                                                                                      |
| 1   | 010            | 0  | 0  | 1  | 0  | 0  | 0  | 0  | 0                                                                                      |
| 1   | 011            | 0  | 0  | 0  | 1  | 0  | 0  | 0  | 0                                                                                      |
| 1   | 100            | 0  | 0  | 0  | 0  | 1  | 0  | 0  | 0                                                                                      |
| 1   | 101            | 0  | 0  | 0  | 0  | 0  | 1  | 0  | 0                                                                                      |
| 1   | 110            | 0  | 0  | 0  | 0  | 0  | 0  | 1  | 0                                                                                      |
| 1   | 111            | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 1                                                                                      |

### VHDL Source Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity demux_1_to_8_beh is
    Port (
        din : in  STD_LOGIC;
        sel : in  STD_LOGIC_VECTOR(2 downto 0);
        dout : out STD_LOGIC_VECTOR(7 downto 0)
    );
end demux_1_to_8_beh;

architecture Behavioral of demux_1_to_8_beh is
begin
    process(din, sel)
    begin
        dout <= (others => '0');
        if din = '1' then
            case sel is
                when "000" => dout(0) <= '1';
                when "001" => dout(1) <= '1';
                when "010" => dout(2) <= '1';
```

```

        when "011" => dout(3) <= '1';
        when "100" => dout(4) <= '1';
        when "101" => dout(5) <= '1';
        when "110" => dout(6) <= '1';
        when "111" => dout(7) <= '1';
        when others => dout <= (others => '0');
    end case;
end if;
end process;
end Behavioral;

```

## **VHDL Test Bench Code:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity tb_demux_truth_table is
end tb_demux_truth_table;

architecture Test of tb_demux_truth_table is
    signal din : STD_LOGIC := '0';
    signal sel : STD_LOGIC_VECTOR(2 downto 0) := (others => '0');
    signal dout : STD_LOGIC_VECTOR(7 downto 0);

    -- Use this to switch between behavior/dataflow
    component demux_1_to_8_beh
        Port (
            din : in STD_LOGIC;
            sel : in STD_LOGIC_VECTOR(2 downto 0);
            dout : out STD_LOGIC_VECTOR(7 downto 0)
        );
    end component;

begin
    uut: demux_1_to_8_beh
        port map (
            din => din,
            sel => sel,
            dout => dout
        );

    stimulus: process
    begin
        -- Test: DIN = 1 with SEL from 000 to 111
        din <= '1';
        for i in 0 to 7 loop
            sel <= std_logic_vector(to_unsigned(i, 3));

```

```


        wait for 10 ns;
    end loop;

    -- Test: DIN = 0 with SEL from 000 to 111
    din <= '0';
    for i in 0 to 7 loop
        sel <= std_logic_vector(to_unsigned(i, 3));
        wait for 10 ns;
    end loop;


    wait;
end process;
end Test;

```

### **Block Diagram:**

 

### **Circuit Diagram:**

 

## Test Bench Waveform:

